

## Assignment–2

200856-Sandeep Kumar Bijarinia

200562-Rishwan Reddy

200530-Kuldeep Singh Chouhan

### Question 1

A carry-look-ahead adder improves speed by reducing the amount of time required to determine carry bits. The carry-lookahead adder calculates one or more carry bits before the sum, which reduces the wait time to calculate the result of the larger-value bits of the adder, in the ripple carry adder the next computation of the sum bit has to wait for the previous bit to complete which increases the duration of computation.

All 1 bit adders calculate their results and simultaneously the next carry is calculated

Analyzing the below truth table we can deduce the formula of the carry of bit  $i^{\text{th}}$

$$C_i = A_i \wedge B_i + ((A_i \oplus B_i) \wedge C_{i-1})$$

Here,  $A_i$  denotes  $i^{\text{th}}$  bit of A

Using this table we can find the carry of all bits simultaneously


A	B	$C_{i-1}$	$C_i$
0	0	x	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	x	1

We, will use  $P_i = A_i \wedge B_i$  and  $Q_i = A_i \oplus B_i$

and  $C_i = P_i + Q_i \cdot C_{i-1}$

We, will recursively call above formula to get the value of Carry after each stage.

 The implementation can be understood by the help of an abstract circuit diagram given below.



## Question 2

8-bit Johnson Counter, is a counter which uses D-Flip Flops (DFFs) one after another where output from previous DFF is used as input for next DFF, the only change being at the last DFF where negation of last output is fed as input for the first DFF, and the loop continues.

So, there would be a pattern as 00000000, 10000000, 11000000, 11100000, 11110000, etc.

### TRUTH TABLE

State	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub>	Q <sub>5</sub>	Q <sub>6</sub>	Q <sub>7</sub>
0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
2	1	1	0	0	0	0	0	0
3	1	1	1	0	0	0	0	0
4	1	1	1	1	0	0	0	0
5	1	1	1	1	1	0	0	0
6	1	1	1	1	1	1	0	0
7	1	1	1	1	1	1	1	0
8	1	1	1	1	1	1	1	1
9	0	1	1	1	1	1	1	1
10	0	0	1	1	1	1	1	1
11	0	0	0	1	1	1	1	1
12	0	0	0	0	1	1	1	1
13	0	0	0	0	0	1	1	1
14	0	0	0	0	0	0	1	1
15	0	0	0	0	0	0	1	1
16	0	0	0	0	0	0	0	1

This can be illustrated using DFFs as shown below.

